

Example #1: A 10 ampere current flows through a wire in 60 seconds.

Determine:

- a) The amount of charge that moves in 60 seconds.
- b) The number of electrons that pass in 60 seconds.

$$a) \quad I = \frac{q}{t}$$

$$\Rightarrow q = 10(60) = \boxed{6.0 \times 10^2 \text{ C}}$$

$$b) \quad 600 \text{ C} \times \frac{1 e^-}{1.6 \times 10^{-19} \text{ C}}$$

$$= \boxed{3.8 \times 10^{21} e^-}$$



Example #2: If a current of 5.0 A flows for 20 minutes, what charge was transferred?

$$20 \text{ minutes} \times \frac{60 \text{ s}}{1 \text{ min}} = 1200 \text{ s.}$$

$$I = \frac{q}{t} \Rightarrow q = 5.0(1200)$$

$$q = 6.0 \times 10^3 \text{ C}$$

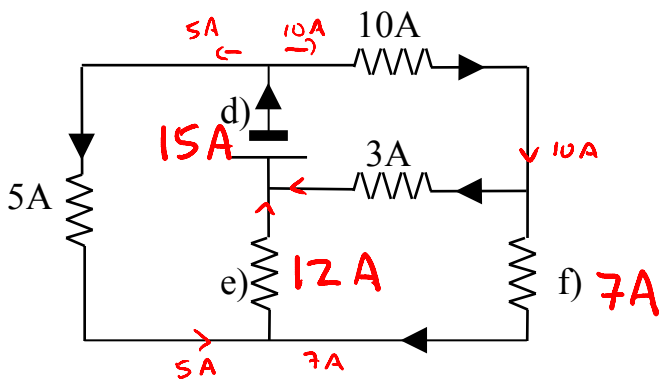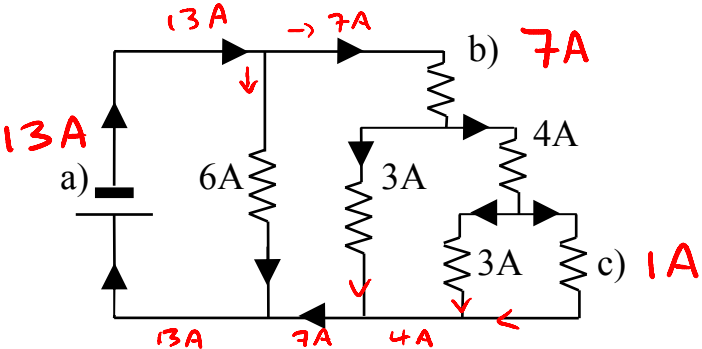Example #3: Determine the unknown currents for each of the following circuits.




Example #4: If a chemical cell gives 600 J of energy to a charge of 50 C, what is the potential difference of this cell?


$$V = \frac{\Delta E_p}{q} = \frac{600}{50}$$

$$V = 12 \text{ V}$$

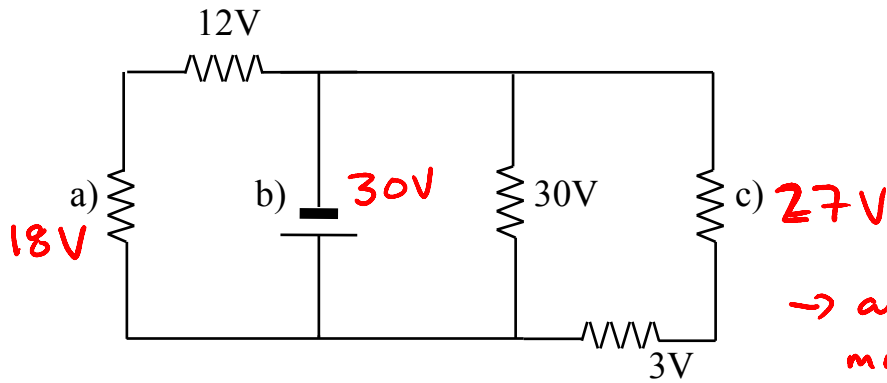Example #5: Determine the unknown voltages for each of the following circuits.



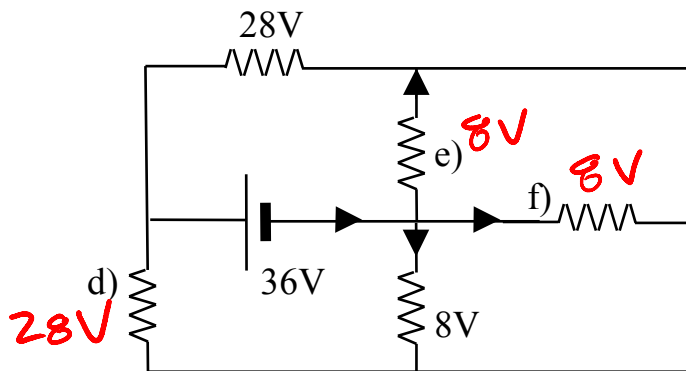\rightarrow all circuit loops must total $30V$



\rightarrow all circuit loops must total $36V$

Example #6: A small light bulb is connected to 3.0 V and will draw 150 mA.

(a) What is the net resistance of the bulb?


(b) If the voltage dropped to 2.0 V, how would the current change?

$$a) \quad 150 \text{ mA} = 0.150 \text{ A}$$

$$R = \frac{V}{I} = \frac{3.0}{0.15} = \boxed{20 \Omega}$$

$$b) \quad I = \frac{V}{R} = \frac{3.0}{20} = \boxed{1.2 \times 10^{-2} \text{ V}}$$

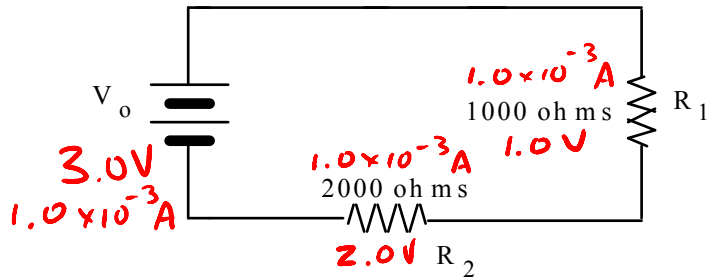Example #7: Consider the following circuit diagram showing two resistors attached in series to a battery of two 1.5 V cells. Determine all unknown voltages, currents and resistances for each apparatus in the circuit.



V_0 = p.d. of 2-1.5 cells in series

Since cells connected in series have their voltages added together, the total voltage,

$$\begin{aligned} V_0 &= 2 \times 1.5 \text{ V} \\ &= 3.0 \text{ V} \end{aligned}$$

$$\rightarrow \text{in series, } R_0 = 1000 + 2000 = 3000 \Omega$$

$$\rightarrow I_0 = \frac{V_0}{R_0} = \frac{3}{3000} = 1.0 \times 10^{-3} \text{ A}$$

\rightarrow in series, I is constant, so

$$I_1 = I_2 = 1.0 \times 10^{-3} \text{ A}$$

Finally,

$$\begin{aligned} V_1 &= I_1 R_1 = .001 (1000) \\ &= 1.0 \text{ A} \end{aligned}$$

$$\begin{aligned} V_2 &= I_2 R_2 = .001 (2000) \\ &= 2.0 \text{ A} \end{aligned}$$

Example #8: Use your calculator to add these resistors in parallel:

(a) 25 Ω , 30 Ω , 50 Ω

(b) 50 Ω , 68 Ω , 270 Ω , 569 Ω


$$a) \frac{1}{R_o} = \frac{1}{25} + \frac{1}{30} + \frac{1}{50}$$

$$R_o = 11 \Omega$$

$$b) R_o = \left[\frac{1}{50} + \frac{1}{68} + \frac{1}{270} + \frac{1}{569} \right]^{-1}$$

$$R_o = 25 \Omega$$

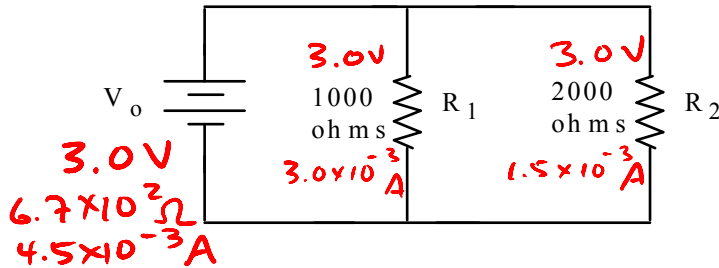Example #9: Consider the following circuit diagram showing two resistors attached in parallel to a battery of two 1.5 V cells. Determine all unknown currents, voltages and resistances.



$$\rightarrow R_0 = \left[\frac{1}{1000} + \frac{1}{2000} \right]^{-1} = 6.7 \times 10^2 \Omega \quad (667)$$

$$\rightarrow I_0 = \frac{V_0}{R_0} = \frac{3.0}{667} = 4.5 \times 10^{-3} A$$


\rightarrow voltage drop across each resistor equals voltage gain by battery, so
 $V_1 = V_2 = 3.0V$

\rightarrow finally,

$$I_1 = \frac{V_1}{R_1} = \frac{3.0}{1000} = 3.0 \times 10^{-3} A$$

$$I_2 = \frac{V_2}{R_2} = \frac{3.0}{2000} = 1.5 \times 10^{-3} A$$

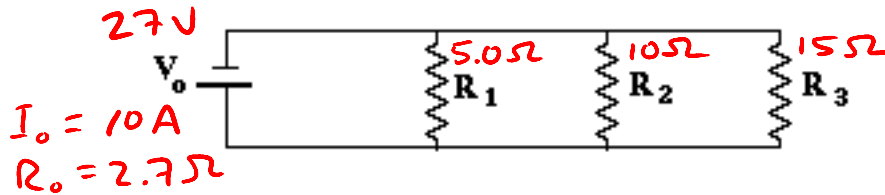Example #10: In this example $R_1 = 5.0 \Omega$, $R_2 = 10 \Omega$ and $R_3 = 15 \Omega$ and the total current is 10 A. Find the current in each branch.



$$\rightarrow \text{first find } R_o = \left[\frac{1}{5} + \frac{1}{10} + \frac{1}{15} \right]^{-1} \\ = 2.7 \Omega$$

$$\rightarrow V_o = I_o R_o = 10(2.7) = 27 \text{ V } (27.3)$$

$$\rightarrow V_1 = V_2 = V_3 = 27 \text{ V}$$

$$\rightarrow \text{finally, } I_1 = \frac{27.3}{5} = 5.5 \text{ A}$$


$$I_2 = \frac{27.3}{10} = 2.7 \text{ A}$$

$$I_3 = \frac{27.3}{15} = 1.8 \text{ A}$$


$$(\text{check: } I_1 + I_2 + I_3 = 10 \text{ A})$$

Example #11: Complete the table for the circuit on the previous page:

R (Ω)	V (V)	I (A)
10	_____	_____
20	_____	_____
30	_____	_____
8	_____	_____
12	_____	_____
15	_____	_____

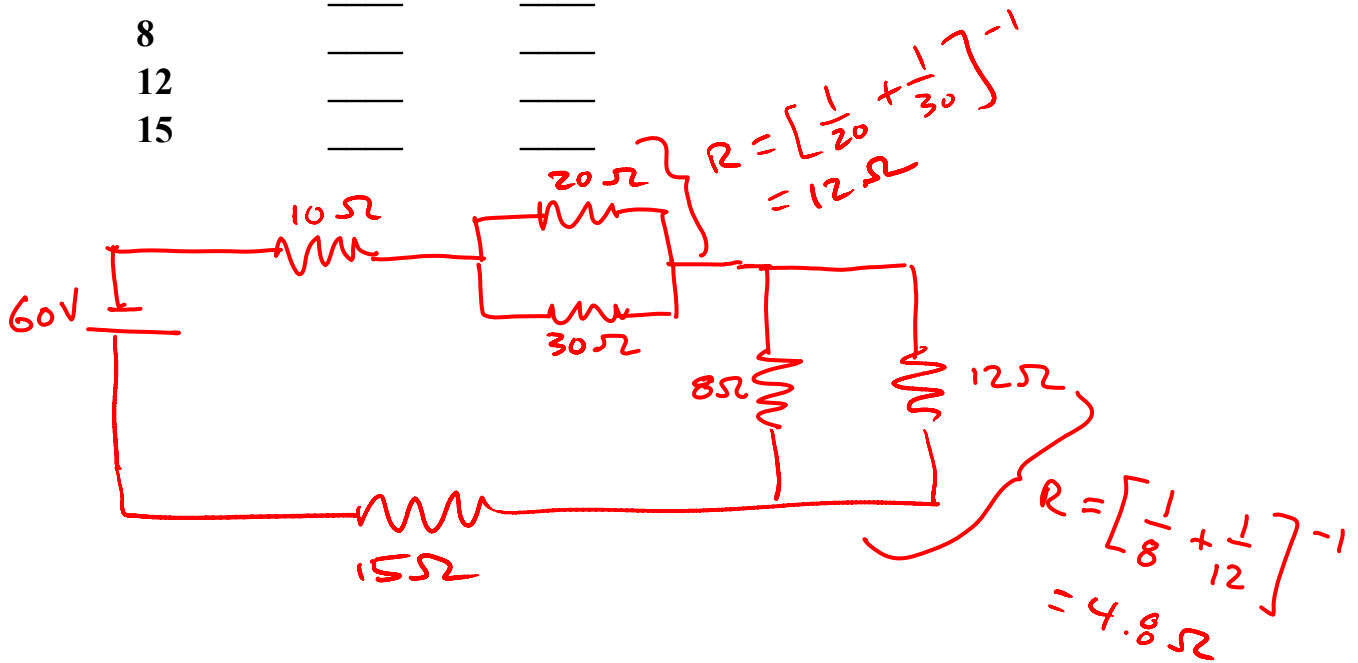

→ Redraw a simplified circuit:

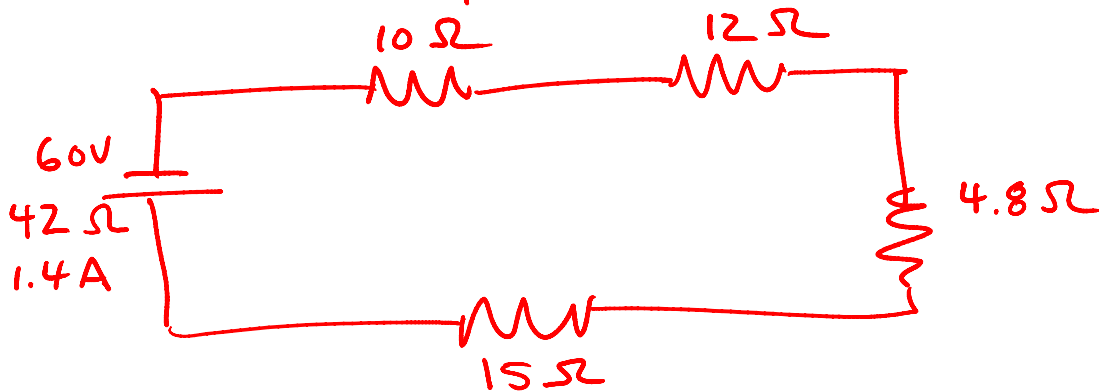


→ $R_o = 10 + 12 + 4.8 + 15 = 42 \Omega$ (41.8)

→ $I_o = \frac{60}{41.8} = 1.4 \text{ A}$ (1.44)

→ analyzing simplified diagram, current through each resistance = 1.44 A
(continued next page)

→ now find voltage drop for each resistance in simplified diagram, using $V = IR$


($I = 1.44 \text{ A}$ for calculations)

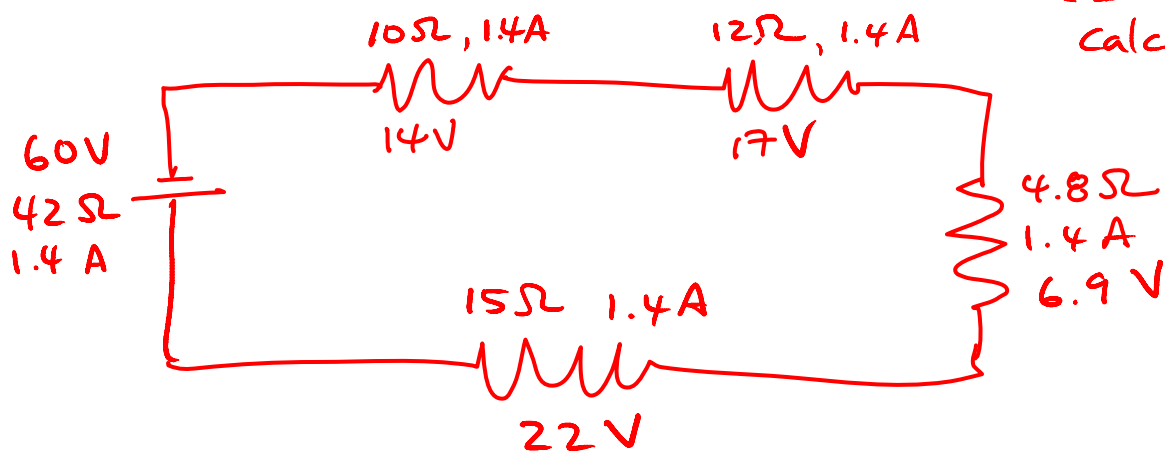

→ at this point, check voltage:


$$14 + 17 + 6.9 + 22 = 59.9 \sim 60 \text{ V } \checkmark$$

→ finally, go back to original diagram:

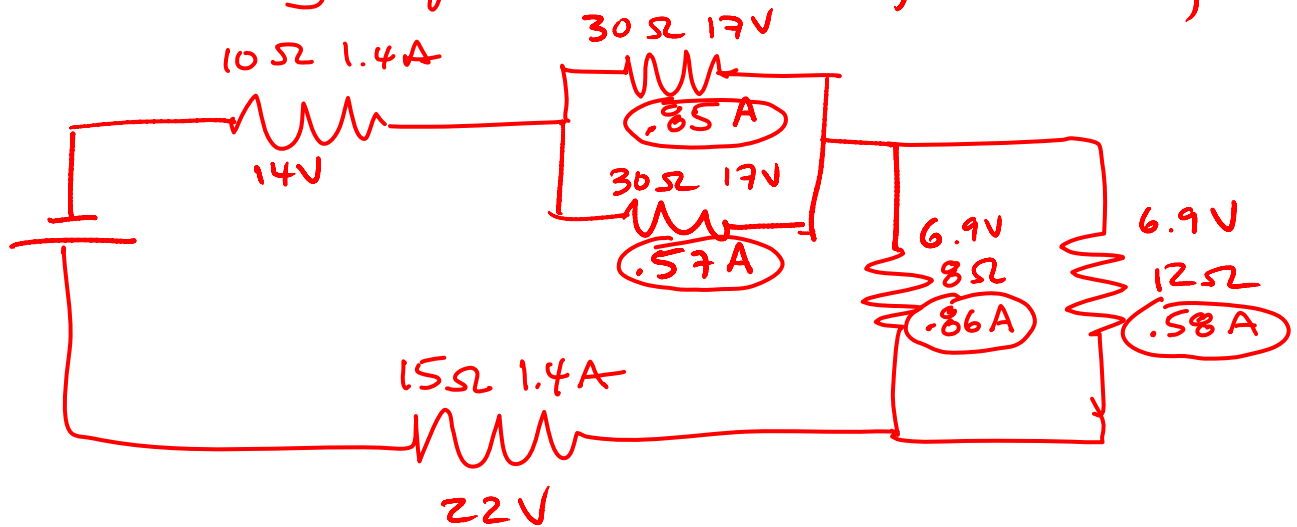


→ using voltage drops, and $I = \frac{V}{R}$, current through parallel resistors can be determined

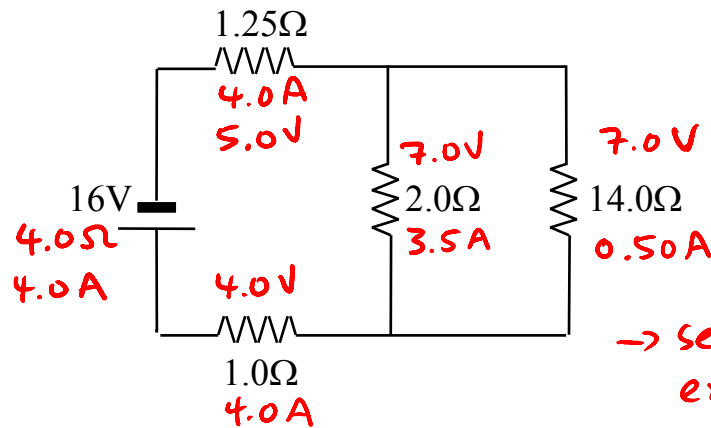Example #12: Calculate all unknown voltages, currents and resistances for the following circuits:



→ see below for explanation

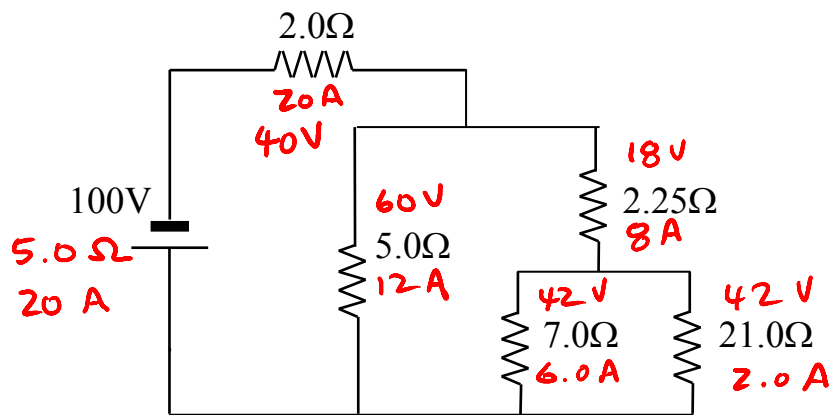

→ see below for explanation

For circuit 1:

→ find R_o , then I_o

→ current through 1.25Ω , 1.0Ω resistors is the same as the battery, so use $V = IR$ to find voltage drops in those resistors

→ finally, use Kirchhoff's Voltage rule to find voltage drop across 2.0Ω , 14Ω resistors, then $I = \frac{V}{R}$ to find current flow in those resistors.

For circuit 2:

→ find R_0 , then I_0

→ current across $2.0\ \Omega$ resistor = I_0 for battery, so use $V = IR$ to find voltage drop in this resistor

→ use Kirchhoff Voltage rule to find drop in $5.0\ \Omega$ resistor, then find current in this resistor

→ use Kirchhoff Current rule to find current flow in $2.25\ \Omega$ resistor, then $V = IR$ to find voltage in this resistor

→ finally, use Kirchhoff Voltage rule to find missing drops in each of $7\ \Omega$, $21\ \Omega$ resistor, and Ohm's Law to find current in each resistor //

Example #13: From the circuit diagram for example 11, calculate the power used by each resistor connected in the circuit.

→ since all voltages + currents are known,
use $P = IV$ to solve for each resistor!

$$10 \Omega \rightarrow 20 \text{ W}$$

$$20 \Omega \rightarrow 15 \text{ W}$$

$$30 \Omega \rightarrow 9.9 \text{ W}$$

$$8.0 \Omega \rightarrow 5.9 \text{ W}$$

$$12 \Omega \rightarrow 4.0 \text{ W}$$

$$15 \Omega \rightarrow 30 \text{ W}$$

Note: power provided by battery
 $= 1.44 \times 60 = 86 \text{ W}$

→ this is equal (within error for rounding) to the total power used by the resistors.

Example #14: Find the cost of operating a kettle for 15 min if it draws 10 A from a standard 120 V outlet, and the cost is 5.5¢/kWh.

$$\rightarrow 15 \text{ min} \times \frac{1 \text{ hr}}{60 \text{ min}} = 0.25 \text{ hr.}$$

$$\rightarrow P = IV = 10(120) = 1200 \text{ W}$$

$$\rightarrow 1200 \text{ W} = 1.2 \text{ kW.}$$

$$\rightarrow \text{energy used: } P = \frac{\Delta E}{t}$$

$$\Delta E = 1.2(0.25) = 0.30 \text{ kW}\cdot\text{h}$$

$$\rightarrow \text{cost} = 0.30 \text{ kW}\cdot\text{h} \times \frac{\$0.055}{\text{kW}\cdot\text{h}}$$

$$= \boxed{\$0.017}$$

Example #15: An electric fan draws 2.0 A of current from a 120 V source. Determine the following:

- (a) the power rating of the fan.
- (b) its electrical resistance.
- (c) the cost of operation of the fan during the month of August, assuming it is run continuously and electric energy costs 10 cents per kilowatt hour.

$$a) P = IV = 2.0(120)$$

$$\boxed{P = 2.4 \times 10^2 \text{ W}}$$

$$b) R = \frac{V}{I} = \frac{120}{2.0} = \boxed{60 \Omega}$$

→ could also use $P = \frac{V^2}{R}$ to solve

$$c) \# \text{ hours} = 31 \text{ days} \times \frac{24 \text{ hr}}{1 \text{ day}}$$

$$= 744 \text{ hr.}$$

power is 0.24 kW

$$P = \frac{\Delta E}{t}, \Delta E = .24(744)$$

$$\Delta E = 178.56 \text{ kW}\cdot\text{h}$$

$$\text{Cost} = 178.56 \text{ kW}\cdot\text{h} \times \frac{\$.10}{\text{kW}\cdot\text{h}}$$

$$\boxed{= \$ 18} \quad (17.86)$$

Example #16: A 6.0 volt motor is used to winch a 0.056 kg mass a vertical distance of 0.65 m in 5.62 sec. What current will the motor draw?

→ use $P = IV$

↳ must find power first

$$P = \frac{\Delta E}{t} = \frac{mg\Delta h}{t}$$

$$= \frac{.056(9.8)(.65)}{5.62}$$

$$= 6.35 \times 10^{-2} \text{ W}$$

$$I = \frac{P}{V} = \frac{.35672}{6.0}$$

$$I = 1.06 \times 10^{-2} \text{ A}$$

Example #17: When a 6.0 V EMF battery was connected to a 15 Ω resistance, a current of 375 mA occurred and the voltmeter reading was 5.625 V.

(a) Find the internal resistance r of this supply.

(b) If this battery is now connected to a 5.0 Ω resistor, what current will flow?

$$a) \quad V_T = \mathcal{E} - I r \quad \text{where } V_T = \text{voltmeter reading}$$

$$5.625 = 6.0 - .375 r$$

$$\boxed{r = 1.0 \Omega}$$

$$b) \quad R_o = 5.0 \Omega$$

$$V_T = \mathcal{E} - I r \quad \text{and} \quad V_T = I R_o$$


$$\text{so } I R_o = \mathcal{E} - I r \Rightarrow \mathcal{E} = I R_o + I r$$

$$\rightarrow I = \frac{\mathcal{E}}{R_o + r} = \frac{6}{5 + 1}$$

$$\boxed{I = 1.0 \text{ A}}$$

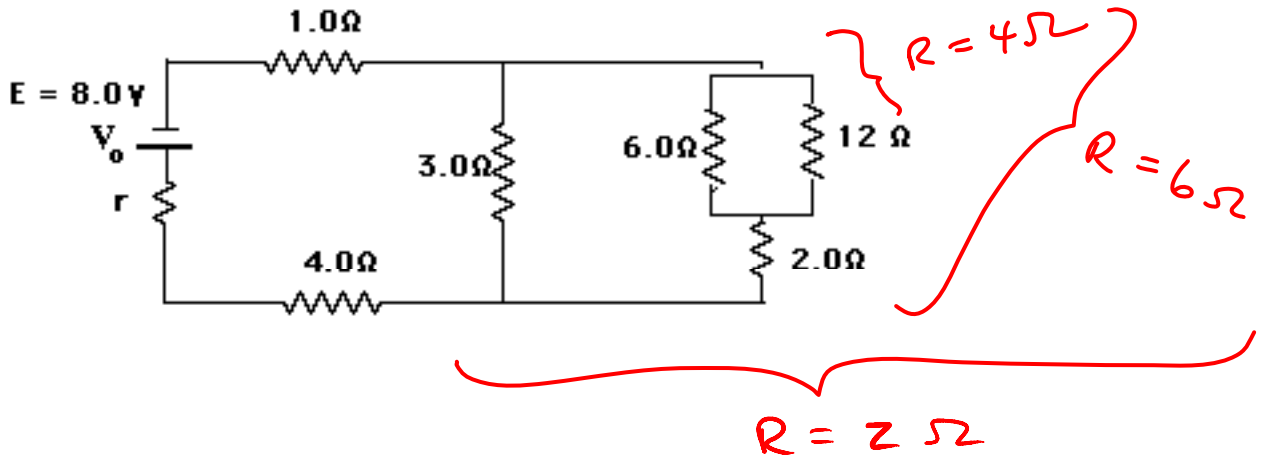Example #18: A battery of EMF 8.0 V and internal resistance $r = 1.0\ \Omega$ is connected to an external circuit as shown. Find:

- the equivalent resistance of the circuit.
- the total current leaving the battery.
- the potential difference between the terminals of the battery.



a) using appropriate techniques to simplify,

$$R_o = 1 + 2 + 4 = \boxed{7.0\ \Omega}$$

b) using $V_T = E - Ir$ and $V_T = IR_o$,

$$I = \frac{E}{R_o + r} = \frac{8.0}{7 + 1} = \boxed{1.0\ \text{A}}$$

c) $V_T = IR_o = 1.0(7.0) = \boxed{7.0\ \text{V}}$