

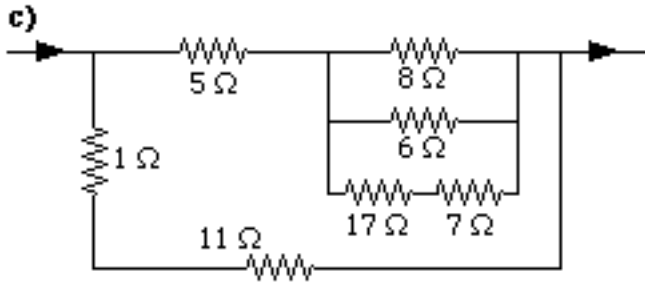
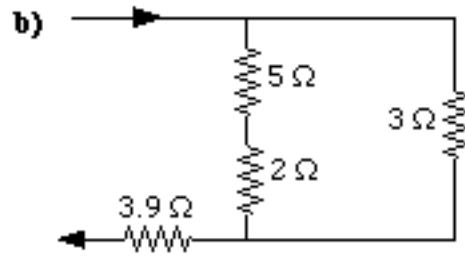
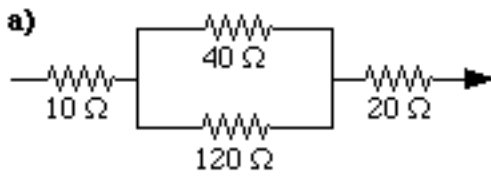
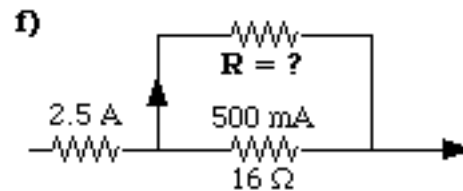
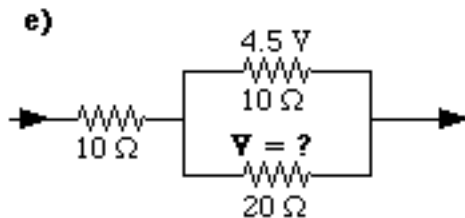
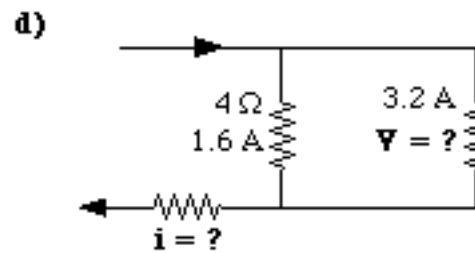
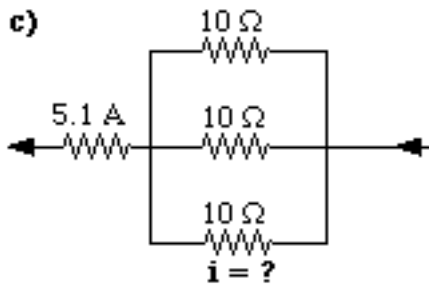




**PHYSICS 12 CIRCUITRY WORKSHEET 2**

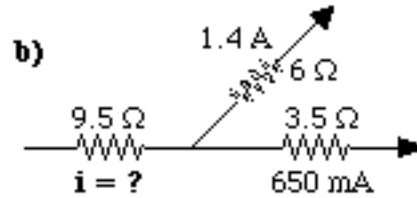1. Calculate the effective resistance of each of the following branches of a circuit.



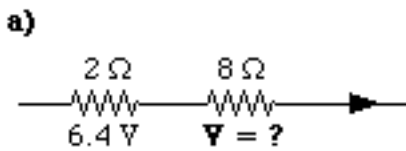2. Determine the value of the indicated quantity for each of the following circuit branches.



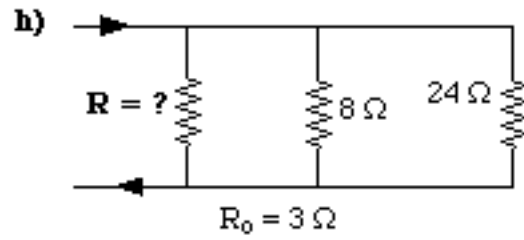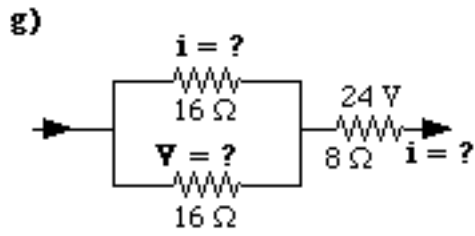

3. Two wires have a combined resistance of  $10\ \Omega$  when in series and  $2.4\ \Omega$  when in parallel. Find the resistance of each wire. (Hint: 2 equations, 2 unknowns)

1. a)  $60\ \Omega$  b)  $6.0\ \Omega$  c)  $4.8\ \Omega$  2. a)  $25.6\text{ V}$  b)  $2.05\text{ A}$  c)  $1.7\text{ A}$  d)  $4.8\text{ A}, 6.4\text{ V}$  e)  $4.5\text{ V}$  f)  $3.2\ \Omega$  g)  $1.5\text{ A}, 24\text{ V}, 3.0\ \Omega$   
 h)  $6\ \Omega$  3.  $6.0\ \Omega, 4.0\ \Omega$